 



Verilog Advanced Question 2

- **Traffic light controller** for a highway (**HW**) and local road (**LR**) intersection
- **HW** has higher priority and should be green as long as possible
- **LR** has a sensor to detect cars on it. When a car is sensed, LR turns green shortly
- Green light is **at least 70** clock cycles and yellow light is **25** clock cycles
- Input: **clk**, **rst_n**, **lr_has_car**; Output: **hw_light[2:0]**, **lr_light[2:0]**
 - **hw_light** & **lr_light**: bits [2:0] represent **Green**, **Yellow**, and **Red**, respectively






Verilog Advanced Question 2 (Con't)

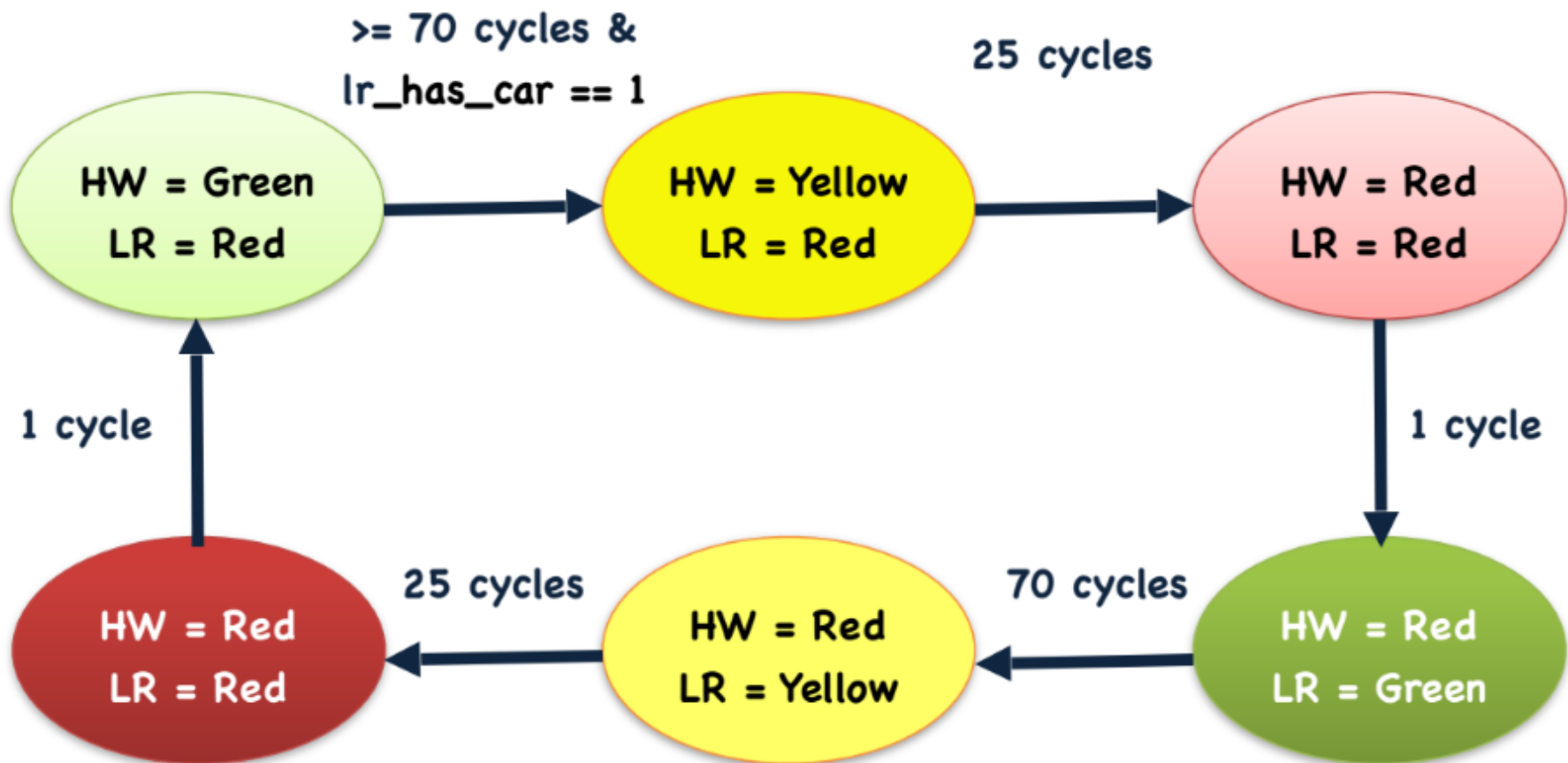- Traffic light controller Finite State Machine
- Please complete the FSM in your report (some arrows are removed intentionally)



Verilog Advanced Question 2 (Con't)

 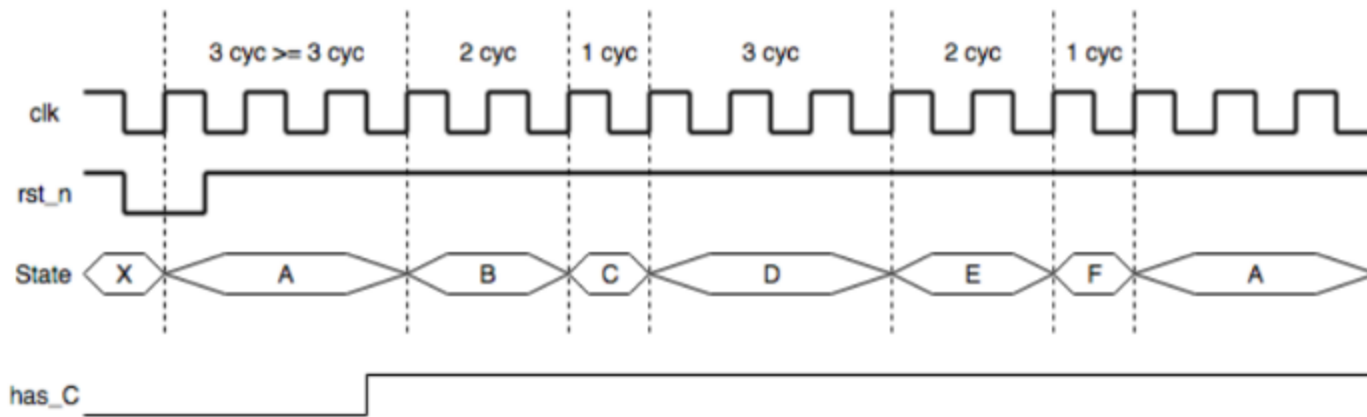 

- A Traffic light controller **"example"** timing diagram is illustrated on the left
- Please make sure that your state transitions follows the timing diagram correctly